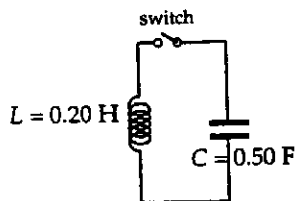


Consider this circuit, which has $C = 0.50 \text{ F}$ and $L = 0.20 \text{ H}$. With the switch open (as drawn here), the capacitor is charged up, using a 2-volt battery. The battery is removed. Then, at time $t = 0$, the switch is closed.



- (a) Immediately before the switch is closed, what's the charge on the capacitor? Call your answer " Q_0 ."
- (b) Set up an equation that could be solved for Q , the charge on the capacitor, as a function of time. Do not solve this equation, unless you want to.
- (c) Sketch a rough graph of i vs. t (after $t = 0$), where i denotes the current through the inductor. This graph need not be numerically accurate. Just worry about the general shape.
- (d) When the charge on the capacitor is $Q_0/2$, what current is flowing through the inductor? Hint: You need not solve the differential equation from part (b). Instead, think about energy.
- (e) The period of oscillation of the LC circuit is $T = 2\pi\sqrt{LC}$. (I figured this out by solving the differential equation from part b.) What is the earliest time, after $t = 0$, when the capacitor has no charge on it?
- (f) Explain, intuitively, why the period of oscillation increases if we raise the inductance, or if we raise the capacitance. It might help you to consider an analogy with a mass on a spring.

a) $Q_0 = CV_0$ (steady state \Rightarrow inductor doesn't matter)

b) Use the Loop Rule

$$\mathcal{E}_L + V_C = 0$$


$$-L \frac{di}{dt} + \frac{Q}{C} = 0$$

But $i = -\frac{dQ}{dt}$ (leaving cap) \Rightarrow $\left[L \frac{d^2Q}{dt^2} + \frac{Q}{C} = 0 \right]$
 This is a DE for Q

c) $L \frac{d^2Q}{dt^2} = -\frac{1}{C} Q$

This is the same equation as for a block on a spring!

Remember

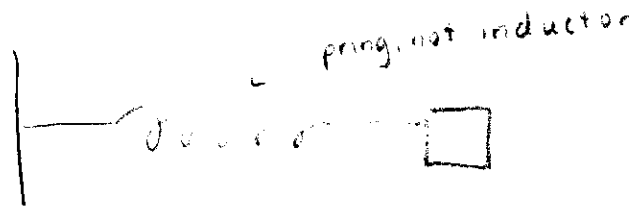

$$F = ma = m \frac{d^2 x}{dt^2} = -kx$$

$$L \frac{d^2 Q}{dt^2} = -\frac{1}{C} Q$$

Same math!
Same solution!


$$\begin{aligned} Q &\leftrightarrow x \\ L &\leftrightarrow m \\ \frac{1}{C} &\leftrightarrow k \end{aligned}$$

Solution: Sinusoid

$$Q = Q_0 \sin(\omega t + \phi)$$

$$I = \frac{dQ}{dt} = Q_0 \omega \cos(\omega t + \phi)$$

Shape looks like:

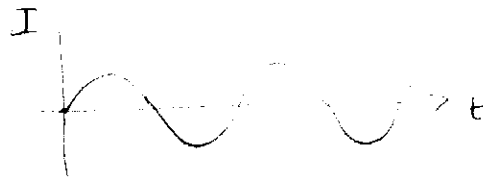

d) Use energy conservation

$$U_C = \frac{1}{2} \frac{Q^2}{C}, \quad U_L = \frac{1}{2} L I^2$$

Note mechanical analogy!

$$\frac{1}{2} kx^2 \quad (\text{like spring PE})$$

$$\frac{1}{2} mv^2 \quad (\text{like KE})$$

when $Q = \frac{Q_0}{2}$

initially when $Q = Q_0$

$$(U_C + U_L)_f = (U_C + U_L)_i$$

we are trying to find this

$$U_{Ci} = \frac{1}{2} \frac{Q_0^2}{C}, \quad U_{Li} = 0; \quad U_{Cf} = \frac{1}{2} \left(\frac{Q_0}{2}\right)^2 \frac{1}{C}, \quad U_{Lf} = \frac{1}{2} L I_f^2$$

$$\frac{1}{2} \frac{Q_0^2}{C} = \frac{1}{2} \left(\frac{Q_0}{2} \right)^2 \frac{1}{C} + \frac{1}{2} L I_f^2$$

Solve for I_f : $I_f^2 = \frac{1}{L} \left[\frac{3 Q_0^2}{4 C} \right]$

When $Q = Q_0$ $I_f = \sqrt{\frac{3 Q_0^2}{4 C L}} = \underline{\underline{2.7 A}}$

e) Our DE is $\frac{d^2 Q}{dt^2} = -\frac{1}{LC} Q$


The sinusoidal solution is for $\omega = \sqrt{\frac{1}{LC}}$

(just as for springs it was)

$$\omega = \sqrt{\frac{k}{m}}$$

So $T = \frac{2\pi}{\omega} = 2\pi\sqrt{LC}$

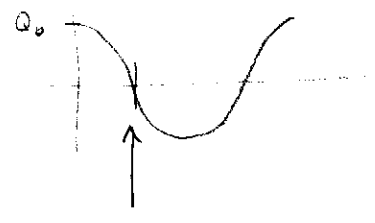The charge swings from Q_0 to 0 to $-Q_0$ to 0 to Q_0 in one period



So the first time it has $Q = 0$ is $\frac{1}{4}$ period

$\Rightarrow t = \frac{1}{4} T = \frac{1}{4} 2\pi\sqrt{LC} = \underline{\underline{0.5 s}}$

f) Mathematically: $T \propto \sqrt{LC}$ so it increases if $L \uparrow, C \uparrow$

mechanical analogy

Intuitively: $\rightarrow L$ is like inertial mass. increasing it makes the circuit respond more slowly, so it sloshes back and forth more slowly

$\rightarrow 1/C$ is like the spring constant.

Increasing C is like decreasing the spring constant, which makes for a (weaker spring)

slower oscillation.

(or: increasing C means more charge can get stuffed on, which means it takes longer to respond)