

A variable-voltage power supply is connected to two inductors, as drawn here. I've used the standard "battery" icon to indicate the power supply. A small picture of a solenoid always denotes an inductor, whether or not the inductor happens to be a solenoid.

The left inductor has inductance $L_1 = 0.4$ henrys. The right inductor has inductance $L_2 = 0.6$ henrys. The power supply is currently set to $V_0 = 10$ volts. Both inductors are in series with resistors of resistance $R = 2 \Omega$.

- (a) Assuming the power supply has been turned on for a long time, what current flows through the left inductor? The right inductor?
- (b) Suddenly, at a moment I'll call $t = 0$, the power supply is abruptly turned down to 0 volts. But current can still flow through its inner workings. Using qualitative reasoning, without doing any calculations, tell me which inductor has more current flowing through it at time $t = 0.1$ s. Explain your reasoning in detail.
- (c) A long time after the power supply is set to 0 volts, what current flows through the right inductor? The left inductor? Why?
- (d) Now write a differential equation that could be solved for i_1 , the current through the left inductor, at arbitrary time t after the power supply is turned to zero. You need not solve the equation, unless you want to. But try to set it up.
- (e) Sketch a rough graph of i_1 vs. time and i_2 vs. time. Let $t = 0$ be the moment the power supply was turned to 0 volts. These graphs need not be numerically accurate.


a) After a long time (in the steady state) there is no current change, so no induced emf

$$\mathcal{E}_L = -L \frac{di}{dt} = 0 \Rightarrow \boxed{\text{Inductor has no effect}}$$

The current is just given by Ohm's Law

$$i_1 = i_2 = \frac{V_0}{R} = \frac{10 \text{ V}}{2 \Omega} = \underline{\underline{5 \text{ A}}}$$

b) At $t = 0$

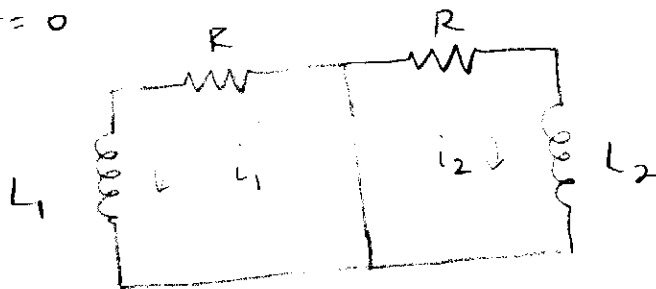

The inductors resist change in current.
 The bigger L , the bigger the opposition, and
 the longer it will take current to settle down

\Rightarrow since $L_2 > L_1$, L_2 will have
 a greater current at any given time

c) At very long times, the current has died
 away completely \Rightarrow $i = 0$ through both

d) Choose current direction and apply
 the loop rule

$$-i_1 R + \mathcal{E}_{L_1} = 0$$

$$-L \frac{di_1}{dt} = \mathcal{E}_{L_1} \Rightarrow \left[i_1 R + L_1 \frac{di_1}{dt} = 0 \right]$$

A D.E. we can solve
 for the current

Let's solve it in order to make part e easier

Separate variables: $\frac{di_1}{i_1} = -\frac{R}{L_1} dt$

Integrate $\int_{i_0}^{i_1} \frac{di_1'}{i_1'} = -\frac{R}{L_1} \int_0^t dt'$

initial current $\rightarrow i_0$


$$\ln i_1 - \ln i_{10} = -\frac{R}{L} t$$

$$\ln\left(\frac{i_1}{i_{10}}\right) = -\frac{R}{L} t$$

$$\frac{i_1}{i_{10}} = e^{-(R/L)t}$$

$$i_1(t) = i_{10} e^{-(R/L)t}$$

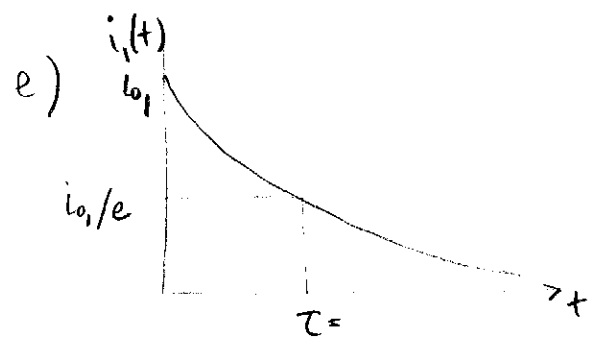This is the current as a function of time after the switch is closed (similar eqn for $i_2(t)$)




$i_1(t) = i_{01}$ at $t = 0$
 $i_1 \rightarrow 0$ as $t \rightarrow \infty$

Time constant $\tau = L/R$

$$i = i_0 e^{-t/\tau}$$

bigger $L \Rightarrow$ bigger τ

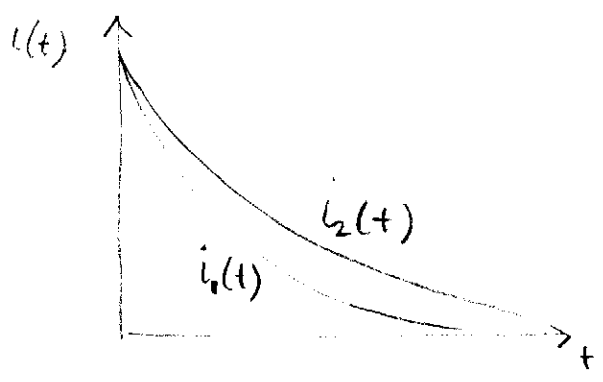So compared to $i_1(t)$, $i_2(t)$ should be more spread out (takes longer to respond)



Mechanical analogy : $L \rightarrow m$
 $R \rightarrow \text{drag}$

$$m \frac{d^2x}{dt^2} = -b v = -b \frac{dx}{dt}$$

Mass with
initial
velocity
under
influence
of drag force

Solution
 $v = v_0 e^{-t(b/m)}$



slows to a stop