

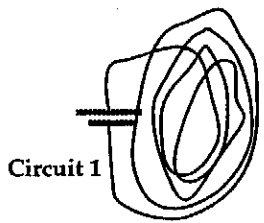


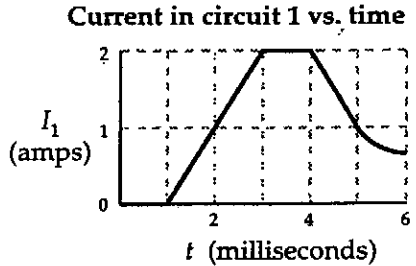Circuit 1 sits next to circuit 2 on a table. Recall from an earlier problem that "mutual inductance" relates the rate of change in current in one system to the EMF induced by that changing current in another system:



$$|\mathcal{E}_{2 \text{ induced}}| = M \frac{dI_1}{dt}$$

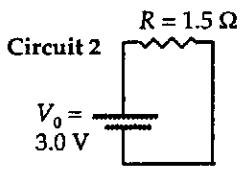where  $I_1$  denotes the current in system 1, and  $\mathcal{E}_{2 \text{ induced}}$  denotes the induced voltage in system 2. Here, the mutual inductance between circuit 1 and circuit 2 is  $M = 1.0 \times 10^{-4}$  henrys. When  $I_1$  increases, the induced EMF in circuit 2 is clockwise. Circuit 2 has negligible self-inductance



By fiddling with the power supply on circuit 1, I make  $I_1$  fluctuate as graphed here. Notice that the time axis is subdivided into milliseconds.

The battery and resistor in circuit 2 have voltage  $V_0 = 3.0$  V and  $R = 1.5 \Omega$ .

- (a) Without using formulas, explain why changing the current in circuit 1 induces an EMF in circuit 2.
- (b) (Very hard) Sketch a rough graph of the current in circuit 2 as a function of time, between  $t = 0$  and  $t = 6$  milliseconds. Your graph need not be numerically accurate.
- (c) What is the current in circuit 2 at time  $t = 2$  milliseconds?
- (d) What is the current in circuit 2 at time  $t = 3.5$  milliseconds?
- (e) At time  $t = 4.5$  milliseconds?
- (f) If circuit 2 were moved farther away from circuit 1, would the mutual inductance go up, go down, or stay the same? Explain your answer.


a) changing current in 1  $\Rightarrow$  changing magnetic flux through 2  $\Rightarrow$  by Faraday's Law, an EMF is induced in 2

b) 
$$Emf_{in\ 2} \propto \frac{d\Phi_{B_{in\ loop\ 2}}}{dt}, \text{ but } \Phi_{B_2} \propto I_1$$

So 
$$EMF_{in\ 2} \propto \frac{dI_1}{dt}$$
 slope of  $I_1$  vs  $t$  graph

The "baseline" current in loop 2 is
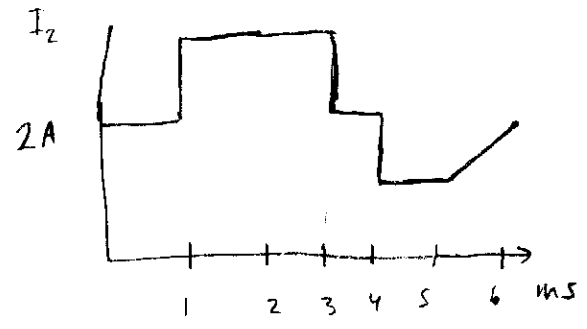
$$I_0 = \frac{3.0}{1.5} = 2\text{ A}, \text{ CW}$$



Between  $t = 1$  and  $t = 3$  ms,  $I_1$  increases CW,  
 $\Phi_{B_1}$  increases in  $\otimes$  dir

so  $\Phi_{B_2}$  increases in  $\odot$  dir

$I_{2ind}$  creates a field to decrease in  $\odot$  dir,

so to increase in  $\otimes$  dir, so CW

flux through 2

This increases  $I_2$ .  $\mathcal{E}_{ind} = \text{constant}$ , since slope of  $I_1$  vs  $t$  is const

Now from  $t = 3$  to  $t = 4$  ms, no change,

so  $I_{ind_2} = 0$  and  $I_2 = 2A$

Between  $t = 4$  and  $t = 5$  ms, steady

decrease in  $I_1 \Rightarrow I_{2ind} = \text{const}$ , and

opposite in direction, so subtracts from 2A

Between  $t = 5$  and  $t = 6$  ms

$I_1$  decreases, with decreasing slope  
 (slope becoming less negative)

$\mathcal{E}_{ind}$  and  $I_{2ind}$  therefore become less negative

c)  $t = 2 \text{ ms}$

$$|\mathcal{E}_2 \text{ ind}| = M \frac{dI_1}{dt} = (1 \times 10^{-4} \text{ H}) \left( \frac{2 - 0}{0.003 - 0.001} \right)$$

$$= 0.10 \text{ V}$$

This adds to  $\mathcal{E}_0 = 3 \text{ V}$

$$\Rightarrow I_2 = \frac{3.1 \text{ V}}{1.5 \Omega} = \underline{\underline{2.07 \text{ A}}}$$

d)  $t = 3.5 \text{ ms}$  No change  $\Rightarrow I_2 = 2 \text{ A}$

e)  $t = 4.5 \text{ ms}$   $\mathcal{E}_{2 \text{ ind}} = -0.10 \text{ V}$

$$I_2 = \frac{2.9 \text{ V}}{1.5 \Omega} = \underline{\underline{1.93 \text{ A}}}$$

f) Mutual inductance would decrease;

$M$  expresses how sensitive a configuration's induced EMF is to changes in current.

Farther  $\Rightarrow$  less flux  $\Rightarrow \frac{d\Phi_B}{dt}$  smaller  $\Rightarrow$  smaller  $M$