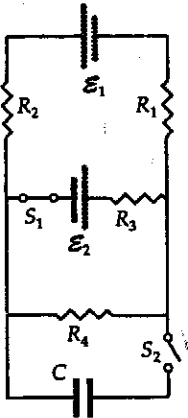


In this circuit, S_1 and S_2 are switches. Current can flow through a switch only when it's "closed." I apologize for this confusing terminology.

The batteries have voltages $\mathcal{E}_1 = 2.0 \text{ V}$ and $\mathcal{E}_2 = 1.5 \text{ V}$. Neither battery has internal resistance. For the resistors, $R_1 = 3.0 \Omega$, $R_2 = 5.0 \Omega$, and $R_3 = 0.50 \Omega$. The resistance R_4 is unknown. The capacitor has capacitance $C = 3.0 \times 10^{-6} \text{ coulomb per volt}$, and is initially uncharged.




When S_1 is closed and S_2 is open, as drawn here, the current through R_4 is measured to be 0.10 amps, leftward.

- Solve for R_4 . Hint: As far as current is concerned, a "dead end" in the circuit might as well not be there at all. Use this insight to simplify the circuit.
- Now S_1 is also opened, so that current flows through neither switch. What's the new current through R_4 ? Explain intuitively why it changed direction.
- [Skip parts (c) through (e) if you don't need to deal with capacitors in circuits] Now, with S_1 still left open, S_2 is closed at time $t = 0$. Immediately after $t = 0$, what's the current through the capacitor? Hint: the capacitor hasn't had time to get charged up by more than a few electron's worth of charge.
- (Very hard) What's the current through R_4 at time $t = 5$ seconds? Hint: Is the capacitor still getting charged up?
- At $t = 5 \text{ s}$, what's the charge on the capacitor?

a) If S_2 open ignore bottom branch.

Circuit is equivalent to:

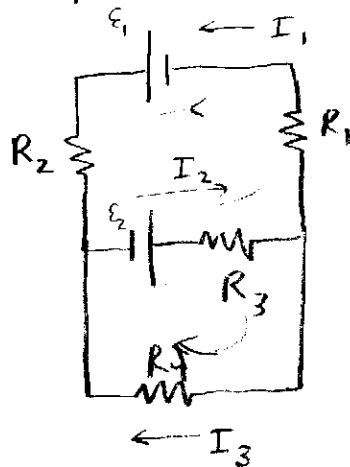

Step 1:

Loops

Step 2:

Currents

Step 3: Junction Rule

$$I_1 + I_3 = I_2 \quad (1)$$

Step 4: Loop Rule: top loop

$$\mathcal{E}_1 - I_1 R_2 + \mathcal{E}_2 - I_2 R_3 - I_1 R_1 = 0 \quad (2)$$

Bottom Loop: $\mathcal{E}_2 - I_2 R_3 - I_3 R_4 = 0$ (3)

(2)

Given $I_3 = 0.1 \text{ A}$


have 3 eqns, 3 unknowns

algebra

Get. $R_4 = 12 \Omega$

b) If S_1 is open, no current can flow through the branch with \mathcal{E}_2, R_3

The circuit becomes equivalent to:

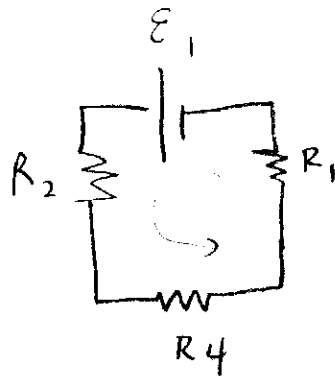

Now it's a simple 1-loop circuit


$$R_{eq} = R_1 + R_2 + R_3$$

$$I = \frac{\mathcal{E}}{R_{eq}} = \frac{2}{3+5+12} = \underline{\underline{0.1 \text{ A}}}$$

Current goes CCW, the way the \mathcal{E}_1 battery wants it to go. Before, there was a competition between 2 batteries.

c) S_2 closed this now becomes an RC charging problem

Equivalent circuit is:

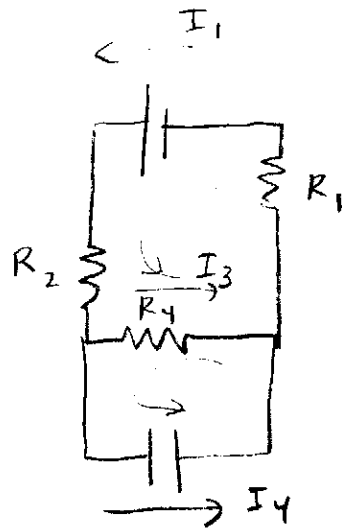

At $t=0$, there's no charge piled up on the capacitor yet, so current flows easily. Treat it with Kirchoff's Rules (I'm relabeling currents - we're looking for I_4)

$$I_1 = I_4 + I_3$$

Top loop: $\mathcal{E}_1 - I_1 R_2 - I_3 R_4 - I_1 R_1 = 0$

Loop with capacitor: $- I_3 R_4 = 0$
 $\Delta V_{cap} = 0$ at $t = 0$
↑ against current


so $I_3 = 0 \Rightarrow$ no current through R_4
 ... because capacitor is like a short!

⇒ Now we have

$$\begin{aligned}
 I_1 &= I_4 \\
 \mathcal{E}_1 - I_1 R_2 - I_1 R_1 &= 0
 \end{aligned}
 \left. \vphantom{\begin{aligned} I_1 &= I_4 \\ \mathcal{E}_1 - I_1 R_2 - I_1 R_1 &= 0 \end{aligned}} \right\} \begin{array}{l} 2 \text{ eqns} \\ 2 \text{ unknowns} \end{array}$$

Get
$$I_4 = \frac{\mathcal{E}_1}{R_1 + R_2} = \frac{2V}{8\Omega} = \underline{\underline{0.25A}}$$
 at $t=0$

with time, it will look like:

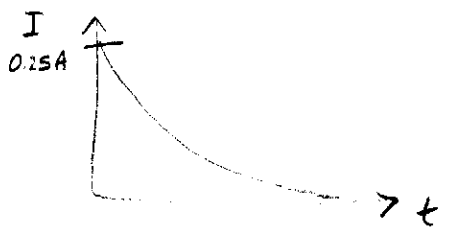

d) We don't really have an equivalent resistance to put into $\tau = RC$, since it's a multi-loop, but order of magnitude: $\tau = RC \sim 5(3 \times 10^{-6}) \sim 15 \times 10^{-6} \sim \underline{\underline{10^{-5} \text{ seconds}}}$

↓

This is very short compared to 5 seconds


So by 5 seconds the capacitor will be fully charged
 When the capacitor is fully charged, there's no current in the capacitor branch

5

The circuit is equivalent to part b.

$$\underline{I = 0.1A} \text{ through } R_4 \text{ as in part b}$$

e) $C = \frac{Q}{V}$

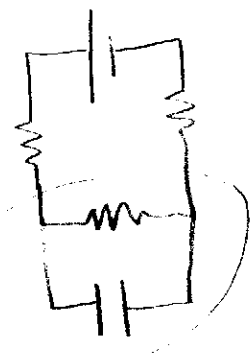

The loop rule holds for this loop,

$$\sum \Delta V_i = 0$$

$$\begin{aligned} \Delta V_{\text{cap}} &= \Delta V_{R_4} = I_4 R_4 \\ &= (0.1A)(12) \end{aligned}$$

$$\Rightarrow Q = (0.1)(12)(3 \times 10^{-6})$$

$$Q = 3.6 \times 10^{-6} \text{ C}$$